 


Switch Level Modeling in Verilog

Sayed Amirhossein Mirhosseini


The nmos and pmos Switches

- To instantiate switch elements:
 - `switch_name [instance_name] (output, input, control);`
- The `instance_name` is optional



		control			
		0	1	x	z
in	0	z	0	L	L
	1	z	1	H	H
	x	z	x	x	x
	z	z	z	z	z

(a) nMOS switch

 

		control			
		0	1	x	z
in	0	0	z	L	L
	1	1	z	H	H
	x	x	z	x	x
	z	z	z	z	z

(b) pMOS switch

Example : The CMOS Inverter

```
module my_not (input x, output f);
```

```
// internal declaration
```

```
supply1 vdd;
```


```
supply0 gnd;
```

```
// NOT gate body
```


```
pmos p1 (f, vdd, x);
```

```
nmos n1 (f, gnd, x);
```

```
endmodule
```

 


(a) Circuit

 


(b) Logic symbol

 Example : CMOS NAND Gate

```
module my_nand (input x, y, output f);  
  supply1 vdd;  
  supply0 gnd;  
  wire a;  
  // NAND gate body  
  pmos p1 (f, vdd, x);  
  pmos p2 (f, vdd, y);  
  nmos n1 (f, a, x);  
  nmos n2 (a, gnd, y);  
endmodule
```




(b) Logic symbol

 


(a) Circuit

What about a NOR gate ?

 


 Any way to reduce the
Number of switches?



 Example : An NMOS NOR Gate


```
module my_nor(input x, y, output f);  
  supply0 gnd;  
  tri1 f;      //To pullup the f node  
  // The nMOS gate body  
  nmos nx (f, gnd, x);  
  nmos ny (f, gnd, y);  
endmodule
```



NMOS NOR Gate


CMOS Switch

 - Is designed to propagate both 0 and 1 well
 - Nmos is only able to propagate 0 well
 - Pmos is only able to propagate 1 well
- To instantiate CMOS switches :
 - `cmos [instance_name] (output, data, ncontrol, pcontrol);`
- The instance_name is optional
- Exactly equivalent to the following :
 `nmos (out, data, ncontrol);`
 `pmos (out, data, pcontrol);`



 Example : A 2-to-1 Multiplexer

```
module my_mux (out, s, i0, i1);  
  output out;  
  input s, i0, i1;  
  //internal wire  
  wire sbar;  
  not (sbar, s);  
  //cmos switches  
  cmos (out, i0, sbar, s);  
  cmos (out, i1, s, sbar);  
endmodule
```



Example : CMOS Flipflop

```
module cff ( q, qbar, d, clk);
```

```
output q, qbar;
```

```
input d, clk;
```

```
//internal nets
```

```
wire e,nclk;
```

```
//the clock inverter
```

```
my_not nt(nclk, clk);
```

```
//the CMOS switches
```

```
cmos (e, d, clk, nclk); //switch C1 closed (e = d) when clk = 1.
```



```
cmos (e, q, nclk, clk); //switch C2 closed (e = q) when clk = 0.
```

```
//instantiate the inverters
```

```
my_not nt1(qbar, e);
```


```
my_not nt2(q, qbar);
```

```
endmodule
```

 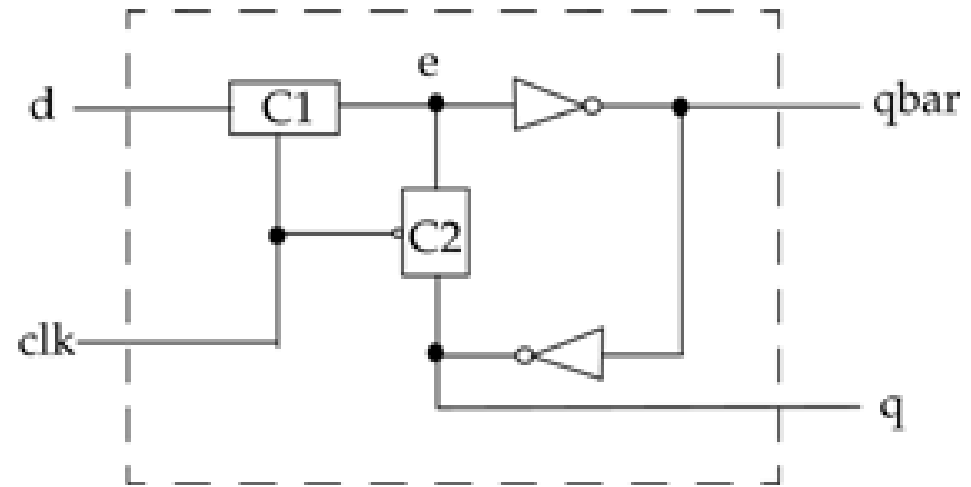


Bidirectional Switches

 
- To instantiate bidirectional switches:
 - `tran [instance_name] (in, out);`
 - `tranif0 [instance_name] (in, out, control);`
 - `tranif1 [instance_name] (in, out, control);`
- `instance_name` is optional



(a) `tran` (`rtran`)

 

(b) `tranif1` (`rtranif1`)

 

(c) `tranif0` (`rtranif0`)

Delay : Unidirectional Switches

- Specify no delay :
 - `mos_sw [instance_name](output, input, ...);`
- Specify propagation delay only :
 - `mos_sw #(prop_delay)[instance_name](output, input, ...);`
- Specify both rise and fall times :
 - `mos_sw #(t_rise, t_fall)[instance_name](output, input, ...);`
- Specify rise, fall, and turn-off times :
 - `mos_sw #(t_rise, t_fall, t_off)[instance_name](output, input, ...);`

Delay : Bidirectional Switches


- These switches do not delay signals passing through them. Instead, they have turn-on and turn-off delays while switching
- Specify no delay :
 - `bdsb name [instance name](in, out, control);`
- Specify a turn-on and turn-off delay :
 - `bdsb name #(t_on_off)[instance name](in, out, control);`
- Specify separately turn-on and turn-off delays :
 - `bdsb name #(t_on, t_off)[instance name](in, out, control);`

Resistive Switches

- MOS, CMOS, and bidirectional switches can be modeled as corresponding resistive devices


MOS	rnmos		rpmos
CMOS	rcmos		
Bidirectional	rtran	rtranif0	rtranif1

Signal Strengths


Strength	Strength0	Strength1	Type	Degree
supply	supply0	supply1	driving	
strong	strong0	strong1	driving	
pull	pull0	pull1	driving	
large	large0	large1	storage	
weak	weak0	weak1	driving	
medium	medium0	medium1	storage	
small	small0	small1	storage	
highz	highz0	highz1	high Z	weakest

Signal Contention

 - **Multiple Signals with Same Value and Different Strength**




 - **Multiple Signals with Opposite Value and Same Strength**



Signal Strength Reduction

 - Non-resistive switches do not reduce the strength except that a supply strength is reduced to a strong strength.
- Resistive switches reduce the signal Strength as follows :



Net Types

- tri
 - Same as wire
 - Used to denote a multi-driver node
- tri0 and tri1
 - used to model resistive pulldown and pullup
 - tri0 net has a value 0 if nothing is driving the net
 - tri1 net has a value 1 if nothing is driving the net
 - The default strength is pull
- supply0 and supply1
 - used to model a power supply
 - have constant logic value and a strength level supply (strongest strength level)

Net Types (cont.)

- trireg
 - used to model nets having capacitance that stores values
 - The default strength for trireg nets is medium and the default value of the is X
 - Driven state
 - At least one driver drives a 0, 1, or x value on the net
 - The value is continuously stored in the trireg net
 - It takes the strength of the driver
 - Capacitive state
 - All drivers on the net have high impedance (z) value
 - The net holds the last driven value
 - The strength is small, medium, or large (default is medium)

triereg Net Charge Decay

- Like all nets, a triereg declaration's delay specification can contain up to three delays :
 - The first two delays specify the simulation time elapsed in a transition to the 1 and 0 logic values in the driven state
 - The third delay :
 - For the other net types shows the time that elapses in a transition to the z logic state
 - For the triereg net type specifies the charge decay time
- The charge decay process ends under one of the following two conditions:
 1. The specified number of time units elapse and the triereg makes a transition from 1 or 0 to x
 2. One of the drivers turn on and propagate a 1, 0 or x into it

Decay Example

```
module capacitor;  
reg data,gate;  
  
triereg (large) #(0,0,50) cap1;  
nmos nmos1 (cap1,data,gate);
```

*triereg declaration
with a charge decay time
of 50 time units*

```
initial  
begin
```

*nmos switch that drives
the triereg*

```
    $monitor("%0d data = %v gate = %v cap1 = %v",  
              $time,data,gate,cap1);
```

```
    data = 1;
```

```
    gate = 1;
```

```
    #10 gate = 0;
```

```
    #30 gate = 1;
```

```
    #10 gate = 0;
```

```
    #100 $finish;
```

```
end
```

*toggles the driver of the
control input to the nmos
switch*

```
endmodule
```

Decay Example (cont.)


```
0 data = St1 gate = St1 cap1 = St1
10 data = St1 gate = St0 cap1 = La1
40 data = St1 gate = St1 cap1 = St1
50 data = St1 gate = St0 cap1 = La1
```

Warning! Time = 100: Charge on node capacitor.cap1 has
decayed [Verilog-DECAY]

"trireg1.v", 4: cap1

```
100 data = St1 gate = St0 cap1 = LaX
```

 *trireg cap1 changes value
to LaX at simulation
time 100*



Charge Sharing Example

```
module triregChargeSharing;
```

```
reg a, b, c;
```

```
wire x;
```

```
trireg (large) y; // declaration with large strength
```

```
trireg (small) z; // declaration with small strength
```

```
not not1 (x, a);
```

```
nmos nmos1 (y, x, b);
```

```
nmos nmos2 (z, y, c); // nmos that drives the trireg
```

Charge Sharing Example (cont.)

initial begin



a = 0; b = 1; c = 1;

#10 c = 0; a = 1;

#10 c = 1; b = 0;

end

endmodule

  

References

- **The Verilog® Hardware Description Language by Donald Thomas and Philip Moorby (2008)**
- **Digital System Designs and Practices: Using Verilog HDL and FPGAs by Ming-Bo Lin (2008)**
- **Verilog HDL (2nd Edition) by Samir Palnitkar (2003)**